

EE 214A Design Project

Sam Fok and Rohit Pidaparthi

November 26, 2012

Parameter	Given Specification	Achieved Specification
Power dissipation	$\leq 3\text{mW}$	1.5667 mW
Small-signal transresistance gain	$\geq 20\text{K}\Omega$	20.148 k Ω
-3dBBandwidth	$\geq 90\text{MHz}$	90.041MHz
Common mode output voltage	-0.5 to 0.5V	-0.1714

Table 1: Specifications.

Part of Circuit	Area in μm^2
Core	132.8
NMOS-bias	40
Bias generator circuit*	8

Table 2: Area of different parts of the circuit. * Without resistor element

Section	% of Core Circuit
NMOS-bias	30.12
Bias generator circuit	6.02

Table 3: Relative area breakdown.

1 Design Outline

Our project was to design the three stage amplifier in figure 2 to the specifications listed in table 1. The common gate stage buffers the input and converts the current signal into a voltage signal, the common source stage amplifies the voltage signal, and the common drain stage buffers the output. Additionally, we designed a current mirror circuit and bias generator circuit to power the amplifier's stages. We first designed the core circuit assuming ideal current sources and then designed the biasing circuits to supply the requisite current for each stage of the amplifier. To simplify the NMOS-Bias circuit dimension calculations, we set the overdrive voltage of the NMOS-Bias circuit to 1V. As a result, we had to design our bias generator circuit to output 1.5V. The bias generator circuit was modeled on the magic battery circuit discussed in lecture.

When designing our core circuit, we started with specifications and technology parameters as inputs. To reduce the number of free parameters we decided set all channel lengths to the minimum length. This also reduced capacitances by minimizing the MOSFET areas, thereby increasing our 3dB bandwidth. Our core circuit design flow is shown in figure 1 and centers on estimating the 3dB bandwidth with ZVTC analysis. We found that the circuit divided into 4 nodes (i.e. time constants) – two nodes between stages and nodes at the input and output. Furthermore, we found that the input and output time constants could be analyzed as functions of two free parameters each: V_{OV} and I_D . Subsequently, the time constants between stages could also be parameterized by two free parameters: A_{V2} and V_{OV2} . It was not sufficient to minimize time constants stage-by-stage as this would leave insufficient current for the last stage analyzed, so we swept over V_{OV1} , I_{D1} , V_{OV3} , I_{D3} , A_{V2} , and V_{OV2} simultaneously and selected instances that met specification. We then scaled our power, bandwidth and gain requirements in Matlab until we found the minimum power design that allowed us to meet the specifications in SPICE.

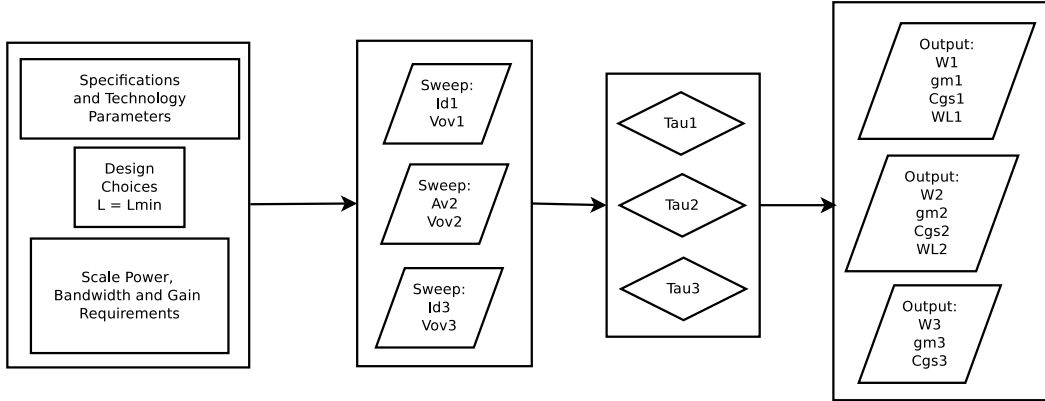


Figure 1: Core Circuit Design Process.

We found a steep bandwidth-power trade off at the common drain stage due to the large output capacitance $C_{out} \sim O(\text{pF})$ and a power-gain tradeoff at the common source stage. The common drain stage required more current and therefore power to counteract the high capacitance of C_{out} . The common source stage was used as a voltage amplifier and the more current it consumed, the higher its gain. To optimize for power, we leveraged the conservative estimate that ZVTC provides for the 3dB bandwidth to relax the constraint on f3dB in our Matlab script so that we could lower the power consumption of our final circuit. We also adjusted our gain requirement until our SPICE result just met the requirements while consuming the least power.

2 Schematic

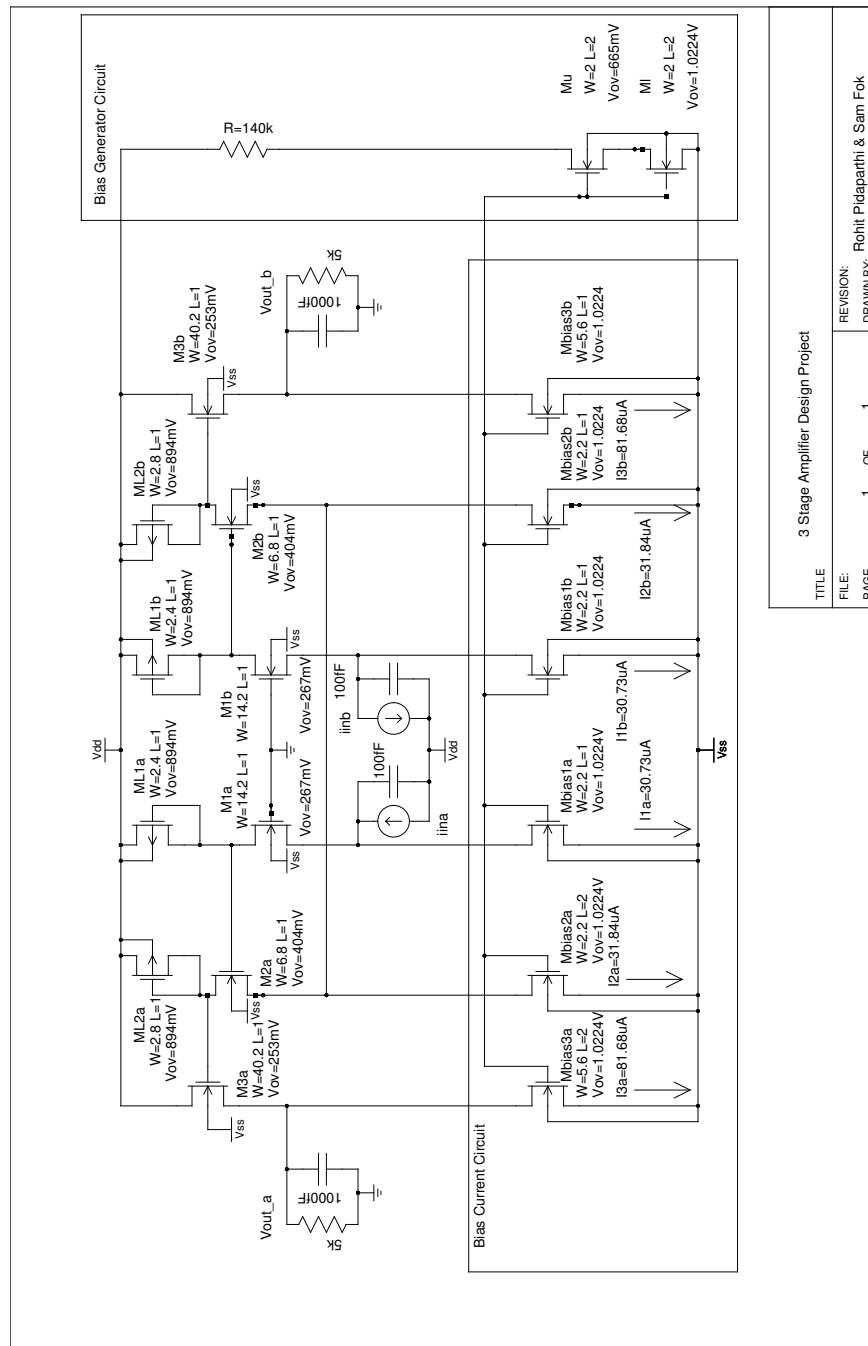


Figure 2: Schematic of our design.

3 Design Parameter Calculations

Our design flow hinges upon estimating the ZVTCs associated with each node of the amplifier. As derived in the appendix,

$$\tau_1 = \frac{V_{ov1}}{2I_{D1}}C_{in} + 1.33 \frac{2}{3} \frac{L_1^2}{\mu_n V_{ov1}} \quad (1)$$

$$\tau_2 = \frac{R_m g_{mL2}}{0.8} (1 + 0.25(1 + A_{v2})) \frac{2}{3} \frac{L_2^2}{\mu_n V_{OV2}} \quad (2)$$

$$\tau_3 = 0.58 A_{v2} \frac{2}{3} \frac{L_2^2}{\mu_n V_{OV2}} + 1.33 \frac{2}{3} \frac{L_{L2}^2}{\mu_p (1 - V_{OV3})} + 0.41 C_{gs3} \frac{1 - V_{OV3}}{2I_{D2}} \quad (3)$$

$$\tau_4 = \frac{1}{1.2} \frac{V_{OV3}}{I_{D3}} C_{out} + \frac{1.33}{1.2} \frac{2}{3} \frac{L_3^2}{\mu_n V_{OV3}} \quad (4)$$

(1) depends only free parameters V_{OV1} and I_{D1} , and (4) takes the same form with V_{OV3} and I_{D3} . Since we picked minimum channel length, the second terms of the sums do not contribute much and τ_1 and τ_4 are minimized by maximizing I_D and minimizing V_{OV} (see Figure 3).

From sweeping I_{D1} and V_{OV1} and picking τ_1 with (1), we extract:

$$\begin{aligned} W_1 &= \frac{2I_{D1}L_1}{KP_n V_{OV1}} \\ g_{m1} &= \frac{2I_{D1}}{V_{OV1}} \\ C_{gs1} &= \frac{\tau_1 g_{m1} - C_{in}}{1.33} \end{aligned}$$

Similarly, sweeping I_{D3} and V_{OV3} and picking τ_4 with (4), we can extract:

$$\begin{aligned} W_3 &= \frac{2I_{D3}L_3}{KP_n V_{OV3}} \\ g_{m3} &= \frac{2I_{D3}}{V_{OV3}} \\ C_{gs1} &= \frac{1.2\tau_4 g_{m3} - C_{out}}{1.33} \end{aligned}$$

With I_{D1} , I_{D3} , and a fixed total power, we can set:

$$\begin{aligned} g_{mL2} &= \frac{2I_{D2}}{V_{OVL2}} \\ W_{L2} &= \frac{2I_{D2}L_{L2}}{KP_p V_{OVL2}^2} \end{aligned}$$

Where $I_{D2} = I_{total} - I_{D1} - I_{D3}$ from the power constraint and $V_{OVL2} = 1 - V_{OV3}$ from the constraint that the common mode output voltage be between -0.5 and $0.5V$ (derivation in appendix). For a given total power, I_{D1} and I_{D3} , I_{D2} is fixed, so (2) and (3) depend only on free parameters A_{v2} and V_{OV2} , so we consider their sum in Figure 4. From V_{OV2} and A_{v2} :

$$\begin{aligned} W_2 &= \frac{2I_{D2}L_2}{KP_n V_{OV2}^2} \\ g_{m2} &= A_{v2} g_{mL2} \\ g_{mL1} &= \frac{0.8A_{v2}}{R_m} \\ V_{OVL1} &= \frac{2I_D}{g_{mL1}} \\ W_{L1} &= \frac{2I_{D1}L_{L1}}{KP_p V_{OVL1}^2} \end{aligned}$$

A minimum power circuit can then be found by incrementally decreasing our total power (hence current) and shrinking our solution space until finding an optimal power circuit.

 


Figure 3: τ_1 and τ_4 take on the same form and both are minimized by maximizing current and minimizing overdrive voltage. We require a large I_{D3} to compensate for the large C_{out} . In addition, V_{OV3} is restricted from being too small by the specification that common mode output voltage be between -0.5 and $0.5V$. Although we could pick I_D and V_{OV} to minimize τ_1 and τ_4 , this would not yield a globally optimal solution as τ_2 and τ_3 are dependent parameters set in picking τ_1 and τ_4 .

 


Figure 4: $\tau_2 + \tau_3$ is a convex surface that increases monotonically with A_{v2} . As A_{v2} increases, the range of feasible V_{OV2} becomes more restricted.

SPICE Results and Comparison with Hand Calculations

Comparisons between hand calculated values and SPICE results are listed in Tables 4 and 5. When we calculated gain, 3dB bandwidth and power consumption by hand, we knew that our 3dB bandwidth would be lower than the SPICE result because ZVTC provides a conservative approximation of 3dB. Therefore, we relaxed the 3dB bandwidth requirement to trade 3dB bandwidth for gain and power. This accounts for the discrepancies between our hand calculations and our final spice bandwidth.

Bias Circuit Calculations

The bias circuit shown in Figure 2 was created using the magic battery technique of Lecture 13. In order to determine the parameters for the bias circuit, we can use the following equation derived in the lecture:

Calculation	Gain($k\Omega$)	BW (Hz)	Power (mW)
Hand	21.949	80.13	1.45
SPICE	20.148	90.041	1.5667
%Difference hand and SPICE	8.2	-12.4	21.5

Table 4: Gain, 3dB bandwidth, and power comparison between hand calculations and SPICE.

	Hand Calculations			Spice Results			% difference		
Mosfet	$g_m(\mu S)$	$I_D(\mu A)$	$V_{OV}(V)$	$g_m(\mu S)$	$I_D(\mu A)$	$V_{OV}(V)$	g_m	I_D	V_{OV}
M1	274	35.6	0.52	230	30.73	0.27	16	13.7	48.5
M2	142	32	0.91	157	31.84	0.40	-10.6	0.6	55.4
M3	795	77.6	0.34	645	81.68	0.25	18.9	-5.3	25.3
ML1	94.9	-35.2	1.5	64.96	-30.73	0.95	31.5	13.7	36.9
ML2	113.3	-32	1.13	71.27	-31.84	0.89	37.1	0.6	21
Mbias1	142.4	35.6	1	60.12	30.73	1.02	57.8	13.7	-2.2
Mbias2	128.2	32	1	62.29	31.84	1.02	51.4	0.6	-2.2
Mbias3	269.5	77.6	1	159.8	81.68	1.02	40.7	-5.3	-2.2

Table 5: Hand calculations vs SPICE simulation results of MOSFET parameters.

$$V_B = \sqrt{\frac{(k+1) \cdot 2I_{bias}}{\frac{W}{L} \cdot KP}} + V_t \quad (5)$$

we can then rearrange to solve for I_{bias} to get:

$$I_{bias} = \frac{(V_B - V_t)^2 \left(\frac{W}{L} \cdot KP\right)}{2 \cdot (k+1)} \quad (6)$$

From project specifications we have the constraint that $W_{min} = 2\mu m$. We then replace W in the equation above with $k \cdot W_{min}$ to get:

$$I_{bias} = \frac{(V_B - V_t)^2 \left(\frac{kW_{min}}{L} \cdot KP\right)}{2 \cdot (k+1)} \quad (7)$$

From this equation, power is minimized if we pick $k=1$ because $\frac{k}{2 \cdot (k+1)} = \frac{1}{4}$ whereas if k increases $\frac{k}{2 \cdot (k+1)} = \frac{1}{2}$. In our design, we chose to create an overvoltage of 1V so we needed to produce a target bias voltage V_B of 1.5V. These choices for k and V_B give us a bias current I_{bias} . We can then use Ohm's law to determine R_B , the resistor we need :

$$R_B = \frac{V_{DD} - V_{ss} - V_{bias}}{I_{bias}} \quad (8)$$

4 Bode Plot

 


Figure 5: Bode Plot

As expected, our hand calculated 3dB bandwidth was lower than the spice result because ZVTC conservatively estimates the bandwidth. Interestingly, the two closely spaced kinks in phase plot around 3g with little corresponding change in the magnitude plot suggest that there is a closely spaced pole-zero pair around 3g.

5 Transient Simulation

 


Figure 6: Transient Simulation. Input is 1MHz, $0.5\mu\text{A}$ differential sine wave. Slightly greater than $20\text{k}\Omega$ gain observed with no distortion.

6 Conclusion

We designed and simulated a differential, three stage amplifier with bias circuitry that met the specifications and minimized power.

We learned to reduce a potentially very high dimensional problem of sizing a multistage circuit to a manageable, lower dimensional space using assumptions about the relative scale of factors and simplifying design choices. Being more familiar with the relative scales and contributions of circuit parameters such as capacitances and conductances would have certainly expedited the design process.

As our first circuit design project, we were tripped up by things we had not encountered before. Having not worked with differential circuits before, we did not discover a bug from not connecting the sources of our differential common source stages in our SPICE deck for days.

7 Appendix

We consider four capacitances for each MOSFET: C_{gs} , C_{gd} , C_{db} , and C_{sb} . For ZVTC analysis, the resistances as seen from each capacitance are listed in (Table 6). To further simplify, we assume that:

$$\begin{aligned} C_{gd}/C_{gs} &= 0.25 \\ C_{db}/C_{gs} &= 0.33 \\ C_{sb}/C_{gs} &= 0.33 \\ g_{mb}/g_m &= 0.2 \end{aligned} \tag{9}$$

We will also use:

$$\frac{C_{gs}}{g_m} = \frac{2}{3} \frac{L^2}{\mu V_{OV}} \tag{10}$$

$$\begin{aligned} R_m &= \frac{1}{g_{mL1}} \frac{g_{m2}}{g_{mL2}} A_{v3} \\ &= \frac{1}{g_{mL1}} \frac{g_{m2}}{g_{mL2}} 0.8 \\ R_m &= \frac{1}{g_{mL1}} A_{v2} 0.8 \end{aligned} \tag{11}$$

Where we assume $A_{v3} = 0.8$ since M_3 is in common drain configuration.

	M_1	M_{L1}	M_2	M_{L2}	M_3
C_{gs}	$\frac{1}{g_{m1}}$	$\frac{1}{g_{mL1}}$	$\frac{1}{g_{mL1}}$	$\frac{1}{g_{mL2}}$	$\frac{R_{out}}{1+g'_m R_{out}} + \frac{1}{6} \frac{1}{g_{mL2}}$
C_{gd}	$\frac{1}{g_{mL1}}$	shorted	$\frac{1}{g_{mL2}} + \frac{1}{g_{mL1}} + A_{v2} \frac{1}{g_{mL1}}$	shorted	$\frac{1}{g_{mL2}}$
C_{db}	$\frac{1}{g_{mL1}}$	$\frac{1}{g_{mL1}}$	$\frac{1}{g_{mL2}}$	$\frac{1}{g_{mL2}}$	$\frac{R_{out}}{1+g'_m R_{out}}$
C_{sb}	$\frac{1}{g_{m1}}$	shorted	shorted	shorted	$\frac{R_{out}}{1+g'_m R_{out}}$

C_{in}	$C_{out} = 2C_L$
$\frac{1}{g_{m1}}$	$\frac{R_{out}}{1+g'_m R_{out}}$

Table 6: Resistances seen by Capacitances. $R_{C_{gd_M2}}$ follows from CS configuration, and $R_{C_{gs_M3}}$ was derived following HW4P3. Also note that $R_{out} = R_L/2$.

From Table 6, we can divide the time constants of the circuit into four groups according to the resistances seen by the capacitors. τ_1 consists of the capacitors that see resistance $\frac{1}{g_{m1}}$:

$$\begin{aligned} \tau_1 &= \frac{1}{g_{m1}} (C_{in} + C_{gs1} + C_{sb1}) \\ &= \frac{1}{g_{m1}} (C_{in} + 1.33C_{gs1}) \\ &= \frac{1}{g_{m1}} C_{in} + 1.33 \frac{C_{gs1}}{g_{m1}} \\ \tau_1 &= \frac{V_{ov1}}{2I_{D1}} C_{in} + 1.33 \frac{2}{3} \frac{L_1^2}{\mu_n V_{ov1}} \end{aligned}$$

The second line follows from (9) and the fourth line follows from (10). τ_2 consists of the capacitors that see resistance $R_{L1} = \frac{1}{g_{mL1}}$:

$$\begin{aligned}
\tau_2 &= \frac{1}{g_{mL1}}(C_{gs2} + (1 + A_{v2})C_{gd2}) \\
&= \frac{1}{g_{mL1}}(1 + 0.25(1 + A_{v2}))C_{gs2} \\
&= \frac{R_m}{A_{v2}0.8}(1 + 0.25(1 + A_{v2}))C_{gs2} \\
&= \frac{R_m g_{mL2}}{0.8}(1 + 0.25(1 + A_{v2}))\frac{C_{gs2}}{g_{m2}} \\
\tau_2 &= \frac{R_m g_{mL2}}{0.8}(1 + 0.25(1 + A_{v2}))\frac{2}{3}\frac{L_2^2}{\mu_n V_{OV2}}
\end{aligned}$$

The second line follows from (9), the third line follows from (11), and the fifth line follows from (10). τ_3 consists of the capacitors that see resistance $\frac{1}{g_{mL2}}$:

$$\begin{aligned}
\tau_3 &= \frac{1}{g_{mL2}}(C_{db2} + C_{gd2} + C_{gsL2} + C_{dbL2} + C_{gd3} + \frac{1}{6}C_{gs3}) \\
&= \frac{1}{g_{mL2}}(0.58C_{gs2} + 1.33C_{gsL2} + 0.41C_{gs3}) \\
&= 0.58A_{v2}\frac{C_{gs2}}{g_{m2}} + 1.33\frac{C_{gsL2}}{g_{mL2}} + 0.41C_{gs3}\frac{V_{OVL2}}{2I_{D2}} \\
&= 0.58A_{v2}\frac{2}{3}\frac{L_2^2}{\mu_n V_{OV2}} + 1.33\frac{2}{3}\frac{L_{L2}^2}{\mu_p V_{OVL2}} + 0.41C_{gs3}\frac{1 - V_{OV3}}{2I_{D2}} \\
\tau_3 &= 0.58A_{v2}\frac{2}{3}\frac{L_2^2}{\mu_n V_{OV2}} + 1.33\frac{2}{3}\frac{L_{L2}^2}{\mu_p(1 - V_{OV3})} + 0.41C_{gs3}\frac{1 - V_{OV3}}{2I_{D2}}
\end{aligned}$$

Note that $V_{OVL2} = 1 - V_{OV3}$ from the constraint that the common mode output voltage be between -0.5 and $0.5V$. If we set $V_{out} = 0V$, we have that $V_{sb3} = 2.5V$ so $V_t(V_{sb3}) = V_{t0} + \gamma(\sqrt{2\phi_f + V_{sb3}} - \sqrt{2\phi_f}) \approx 1V$ for the given technology parameters

$$\begin{aligned}
V_{OV3} &= V_{gs3} - V_t(V_{sb3}) \\
&= V_{g3} - V_{out} - 1V \\
V_{OV3} &= V_{g3} - 0V - 1V
\end{aligned} \tag{12}$$

$$\begin{aligned}
V_{OVL2} &= V_{sgL2} - V_{tL2} \\
&= V_{DD} - V_{g3} - V_{tL2} \\
&= 2.5V - V_{g3} - 0.5V \\
V_{OVL2} &= 2V - V_{g3}
\end{aligned} \tag{13}$$

Adding (12) to (13) yields

$$V_{OV3} + V_{OVL2} = 1V \tag{14}$$

As $R_{out} = 5k\Omega$ and $\frac{1}{g_{m3}} = O(1k\Omega)$, we can approximate $\frac{R_{out}}{1 + g_{m3}R_{out}}$ with $\frac{1}{g_{m3}}$, so τ_4 follows the same steps as τ_1 :

$$\begin{aligned}
\tau_4 &= \frac{1}{g_{m3}}(C_{out} + C_{gs3} + C_{sb3}) \\
&= \frac{1}{1.2g_{m3}}(C_{out} + 1.33C_{gs3}) \\
&= \frac{1}{1.2}\frac{1}{g_{m3}}C_{out} + \frac{1.33}{1.2}\frac{C_{gs3}}{g_{m3}} \\
\tau_4 &= \frac{1}{1.2}\frac{V_{OV3}}{I_{D3}}C_{out} + \frac{1.33}{1.2}\frac{2}{3}\frac{L_3^2}{\mu_n V_{OV3}}
\end{aligned}$$

```

* Design Problem, ee114/214A- 2012
* Please fill in the specification achieved by your circuit
* before your submit the netlist.
*****
* The specifications that this script achieves are:
* sunetid = rohitpid, samfok
* Power   = 1.5667 mW
* Gain    = 20.148 K
* BandWidth = 90.041 MHz
*****

** Including the model file
.include /usr/class/ee114/hspice/ee114_hspice.sp

* Defining Top level circuit parameters
.param Cin = 100f
.param CL  = 500f
.param RL  = 10K

* defining the supply voltages

vdd vdd 0 2.5
vss vss 0 -2.5

* Defining the input current source

** For ac simulation uncomment the following 2 lines**
Iina      iina      vdd      ac      0.5
Iinb      vdd       iinb     ac      0.5

** For transient simulation uncomment the following 2 lines**
*Iina      iina      vdd      sin(0 0.5u 1e6)
*Iinb      vdd       iinb     sin(0 0.5u 1e6)

* Defining Input capacitance

Cina      vdd       iina      'Cin'
Cinb      vdd       iinb      'Cin'

* Defining the differential load

RL         vouta          voutb          'RL'
CL         vouta          voutb          'CL'

*** Your Trans-impedance Amplifier here ***
**nmos***
*name drain gate source bulk type parameters*
M1a node_1a 0 iina vss nmos114 w=14.2u l=1u
M1b node_1b 0 iinb vss nmos114 w=14.2u l=1u
M2a node_2a node_1a ibias2 vss nmos114 w=6.8u l=1u
M2b node_2b node_1b ibias2 vss nmos114 w=6.8u l=1u
M3a vdd node_2a vouta vss nmos114 w=40.2u l=1u
M3b vdd node_2b voutb vss nmos114 w=40.2u l=1u

**pmos***
*name drain gate source bulk type parameters*
ML1a node_1a node_1a vdd vdd pmos114 w=2.4u l=1u
ML1b node_1b node_1b vdd vdd pmos114 w=2.4u l=1u
ML2a node_2a node_2a vdd vdd pmos114 w=2.8u l=1u
ML2b node_2b node_2b vdd vdd pmos114 w=2.8u l=1u

*** Your Bias Circuitry here ***
**nmos***
*name drain gate source bulk type parameters*
Mbias1a iina nbias vss vss nmos114 w=2.2u l=2u
Mbias1b iinb nbias vss vss nmos114 w=2.2u l=2u

```

```
Mbias2a ibias2 nbias vss vss nmos114 w=2.2u l=2u
Mbias2b ibias2 nbias vss vss nmos114 w=2.2u l=2u
Mbias3a vouta nbias vss vss nmos114 w=5.6u l=2u
Mbias3b voutb nbias vss vss nmos114 w=5.6u l=2u
```

```
*** nmos
*** drain gate source bulk mostype w_value l_value
Mu nbias nbias vx vss nmos114 w=2u l=1u
Ml vx nbias vss vss nmos114 w=2u l=1u
```

```
*Resistors
R vdd nbias 140k
```

```
* defining the analysis
```

```
.op
.option post brief nomod
```

```
** For ac simulation uncomment the following line**
.ac dec 100 100 10g
.measure ac gainmax max vdb(vouta)
.measure ac f3db when vdb(vouta)='gainmax-3'
```

```
** For transient simulation uncomment the following line **
*.tran 0.01u 4u
```

```
.end
```

***** HSPICE -- B-2008.09-SP1 32-BIT (Nov 24 2008) linux *****

* design problem, ee114/214a- 2012

***** operating point information tnom= 25.000 temp= 25.000 *****

***** operating point status is all simulation time is 0.

node	=voltage	node	=voltage	node	=voltage
+0:ibias2	=-345.1616m	0:iina	= -1.1166	0:iinb	= -1.1166
+0:nbias	=-977.6485m	0:node_1a	= 1.0540	0:node_1b	= 1.0540
+0:node_2a	= 1.1064	0:node_2b	= 1.1064	0:vdd	= 2.5000
+0:vouta	=-171.4282m	0:voutb	=-171.4282m	0:vss	= -2.5000
+0:vx	= -2.2270				

**** voltage sources

```
subckt
element 0:vdd      0:vss
volts    2.5000    -2.5000
current  -313.3478u 313.3478u
power    783.3695u 783.3695u
```

total voltage source power dissipation= 1.5667m watts

**** current sources

```
subckt
element 0:iina     0:iinb
volts    -3.6166    3.6166
current   0.         0.
power    0.         0.
```

total current source power dissipation= 0. watts

**** resistors

```
subckt
element 0:rl       0:r
r value   10.0000k 140.0000k
v drop    832.6673a 3.4776
current   8.327e-20 24.8403u
power     0.       86.3860u
```

**** mosfets

```
subckt
element 0:m1a      0:m1b      0:m2a      0:m2b      0:m3a      0:m3b
model   0:nmos114. 0:nmos114. 0:nmos114. 0:nmos114. 0:nmos114. 0:nmos114.
region  Saturati   Saturati   Saturati   Saturati   Saturati   Saturati
id      30.7312u   30.7312u   31.8399u   31.8399u   81.6826u   81.6826u
ibs     -13.8338f  -13.8338f  -21.5484f  -21.5484f  -23.2857f  -23.2857f
ibd     -35.5398f  -35.5398f  -36.0644f  -36.0644f  -50.0000f  -50.0000f
vgs     1.1166     1.1166     1.3991     1.3991     1.2779     1.2779
vds     2.1706     2.1706     1.4516     1.4516     2.6714     2.6714
vbs     -1.3834    -1.3834    -2.1548    -2.1548    -2.3286    -2.3286
vth     849.9200m  849.9200m  994.7223m  994.7223m  1.0246     1.0246
vdsat   266.6980m  266.6980m  404.4160m  404.4160m  253.2614m  253.2614m
vod     266.6980m  266.6980m  404.4160m  404.4160m  253.2614m  253.2614m
beta    864.1122u  864.1122u  389.3546u  389.3546u  2.5470m    2.5470m
gam eff 600.0000m  600.0000m  600.0000m  600.0000m  600.0000m  600.0000m
```

gm	230.4570u	230.4570u	157.4612u	157.4612u	645.0458u	645.0458u
gds	2.5250u	2.5250u	2.7804u	2.7804u	6.4462u	6.4462u
gmb	46.7893u	46.7893u	27.4807u	27.4807u	109.4054u	109.4054u
cdtot	15.1944f	15.1944f	8.1767f	8.1767f	37.8570f	37.8570f
cgtd	36.4525f	36.4525f	17.3665f	17.3665f	103.1510f	103.1510f
cstot	39.0998f	39.0998f	19.2848f	19.2848f	103.5813f	103.5813f
cbtot	18.6108f	18.6108f	10.3140f	10.3140f	40.2499f	40.2499f
cgs	28.8734f	28.8734f	13.8267f	13.8267f	81.7403f	81.7403f
cgd	7.1945f	7.1945f	3.4303f	3.4303f	20.4293f	20.4293f

subckt						
element	0:ml1a	0:ml1b	0:ml2a	0:ml2b	0:mbias1a	0:mbias1b
model	0:pmos114.	0:pmos114.	0:pmos114.	0:pmos114.	0:nmos114.	0:nmos114.
region	Saturati	Saturati	Saturati	Saturati	Saturati	Saturati
id	-30.7312u	-30.7312u	-31.8399u	-31.8399u	30.7312u	30.7312u
ibs	0.	0.	0.	0.	0.	0.
ibd	14.4602f	14.4602f	13.9356f	13.9356f	-13.8338f	-13.8338f
vgs	-1.4460	-1.4460	-1.3936	-1.3936	1.5224	1.5224
vds	-1.4460	-1.4460	-1.3936	-1.3936	1.3834	1.3834
vbs	0.	0.	0.	0.	0.	0.
vth	-500.0000m	-500.0000m	-500.0000m	-500.0000m	500.0000m	500.0000m
vdsat	-946.0234m	-946.0234m	-893.5570m	-893.5570m	1.0224	1.0224
vod	-946.0234m	-946.0234m	-893.5570m	-893.5570m	1.0224	1.0224
beta	68.6761u	68.6761u	79.7549u	79.7549u	58.8043u	58.8043u
gam eff	600.0000m	600.0000m	600.0000m	600.0000m	600.0000m	600.0000m
gm	64.9692u	64.9692u	71.2655u	71.2655u	60.1187u	60.1187u
gds	2.6849u	2.6849u	2.7946u	2.7946u	1.4372u	1.4372u
gmb	21.7913u	21.7913u	23.9032u	23.9032u	20.1644u	20.1644u
cdtot	4.7373f	4.7373f	5.3027f	5.3027f	4.5877f	4.5877f
cgtd	6.1194f	6.1194f	7.1407f	7.1407f	9.0141f	9.0141f
cstot	9.9800f	9.9800f	11.2934f	11.2934f	12.6067f	12.6067f
cbtot	8.6553f	8.6553f	9.5262f	9.5262f	8.2778f	8.2778f
cgs	4.8800f	4.8800f	5.6934f	5.6934f	7.8467f	7.8467f
cgd	1.2106f	1.2106f	1.4120f	1.4120f	1.1187f	1.1187f

subckt						
element	0:mbias2a	0:mbias2b	0:mbias3a	0:mbias3b	0:mu	0:ml
model	0:nmos114.	0:nmos114.	0:nmos114.	0:nmos114.	0:nmos114.	0:nmos114.
region	Saturati	Saturati	Saturati	Saturati	Saturati	Linear
id	31.8399u	31.8399u	81.6826u	81.6826u	24.8403u	24.8403u
ibs	0.	0.	0.	0.	-2.7295f	0.
ibd	-21.5484f	-21.5484f	-23.2857f	-23.2857f	-15.2235f	-2.7295f
vgs	1.5224	1.5224	1.5224	1.5224	1.2494	1.5224
vds	2.1548	2.1548	2.3286	2.3286	1.2494	272.9544m
vbs	0.	0.	0.	0.	-272.9544m	0.
vth	500.0000m	500.0000m	500.0000m	500.0000m	584.8448m	500.0000m
vdsat	1.0224	1.0224	1.0224	1.0224	664.5523m	272.9544m
vod	1.0224	1.0224	1.0224	1.0224	664.5523m	1.0224
beta	60.9258u	60.9258u	156.3000u	156.3000u	112.4940u	102.7295u
gam eff	600.0000m	600.0000m	600.0000m	600.0000m	600.0000m	600.0000m
gm	62.2876u	62.2876u	159.7935u	159.7935u	74.7581u	28.0405u
gds	1.4372u	1.4372u	3.6582u	3.6582u	2.2081u	79.4033u
gmb	20.8919u	20.8919u	53.5964u	53.5964u	21.6516u	9.4051u
cdtot	4.2679f	4.2679f	7.6382f	7.6382f	4.2969f	7.2545f
cgtd	9.0245f	9.0245f	22.9775f	22.9775f	5.1045f	6.5858f
cstot	12.6067f	12.6067f	27.4534f	27.4534f	8.2756f	8.1180f
cbtot	7.9476f	7.9476f	12.3624f	12.3624f	7.5284f	8.8311f
cgs	7.8467f	7.8467f	19.9734f	19.9734f	4.0667f	3.5180f
cgd	1.1291f	1.1291f	2.8800f	2.8800f	1.0077f	3.0456f

* design problem, ee114/214a- 2012

```
***** ac analysis tnom= 25.000 temp= 25.000 *****
gainmax= 8.0064E+01 at= 1.2882E+04
          from= 1.0000E+02 to= 1.0000E+10
f3db= 9.0041E+07
```

***** job concluded

```
***** HSPICE -- B-2008.09-SP1 32-BIT (Nov 24 2008) linux *****
*****
```

* design problem, ee114/214a- 2012

```
***** job statistics summary tnom= 25.000 temp= 25.000 *****
```

***** HSPICE Threads Information *****

```
Command Line Threads Count:      0
Available CPU Count:             8
Actual Model Evaluation(Load) Threads Count: 1
Actual Solver Threads Count:     1
```

***** Circuit Statistics *****

```
# nodes      =      14 # elements   =      27
# resistors  =       2 # capacitors =       3 # inductors   =       0
# mutual_inds =       0 # vccs      =       0 # vcvs       =       0
# cccs       =       0 # ccvs      =       0 # volt_srcs  =       2
# curr_srcs  =       2 # diodes    =       0 # bjts       =       0
# jfets      =       0 # mosfets   =      18 # U elements =       0
# T elements =       0 # W elements =       0 # B elements =       0
# S elements =       0 # P elements =       0 # va device  =       0
```

***** Runtime Statistics (seconds) *****

```
analysis      time      # points  tot. iter  conv.iter
op point      0.00         1         7
ac analysis    0.02       801       801
readin        0.00
errchk        0.00
setup         0.00
output        0.00
```

```
total memory used      184 kbytes
total cpu time         0.02 seconds
total elapsed time     0.09 seconds
job started at        01:51:59 11/26/2012
job ended at          01:51:59 11/26/2012
```